

One of the most crucial drawbacks of the 555 astable multivibrator is that the generated frequency and the duty cycle are interdependent. When you change one, the other changes too. Usually manual control is set up through a variable resistance, because wide-range variable capacitors are expensive and hard to find. Unfortunately, the same resistances in the circuit control both the output frequency and the duty cycle of the generated waveform.

The circuit shown in Fig. 3-10 shows a neat way around this problem, using both sections of a 556 dual-timer IC. The first stage is an astable multivibrator with a manually variable frequency through potentiometer R2. The value of resistor R3 is relatively small, so the duty

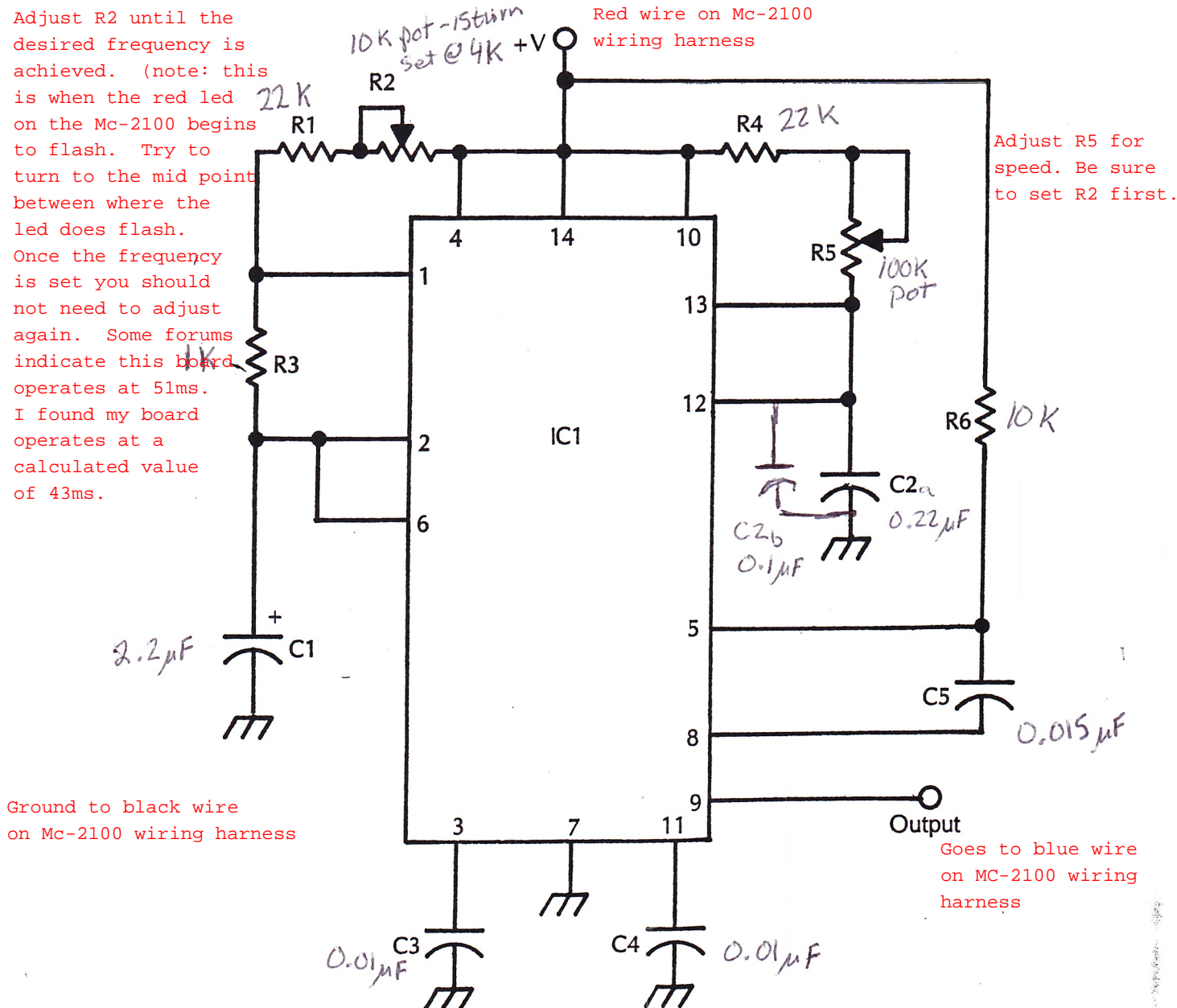


Fig. 3-10 Project 16: Variable-frequency/variable-duty-cycle rectangle-wave generator.

Astable Multivibrator - first half of 556 dual timer

$$T(\text{frequency}) = \frac{1}{0.693 \times C1 \times (Ra + 2R3)}$$

Working Scenario

Factor		0.693
C1	2.2 μ F	0.0000022
R1	22 k	22,000
R2	10 k pot	4,000
Ra = R1+R2		26,000
R3	1.0k	1000
Frequency	=	23.43
Milliseconds	=	42.69

Monostable Multivibrator - sencond half of 556 dual timer

$$T(\text{pulse width}) = 1.1 \times Rb \times C2$$

Factor		1.1
C2a + C2b	0.33 μ F	0.00000033
R4	22 k	22,000
R5	100k pot	50,000
Rb = R4+R5		72,000
Pulse width (seconds)		0.0261
Downtime (seconds)		0.0166
		<hr/> 0.0427 <hr/>
Duty cycle		61.2%

Parts List

IC1	556 dual-timer	R1	22 k
C1	2.2 μ F, 35 volt electrolytic	R2	10 k pot @ 4 k
C2a	0.10 μ F	R3	1.0 k
C2b	0.22 μ F	R4	22 k
C3	0.01 μ F	R5	100 k pot
C4	0.01 μ F	R6	10 k
C5	0.015 uF		

note: c5 Should be 0.001uf; 1nf; or 1000pf