

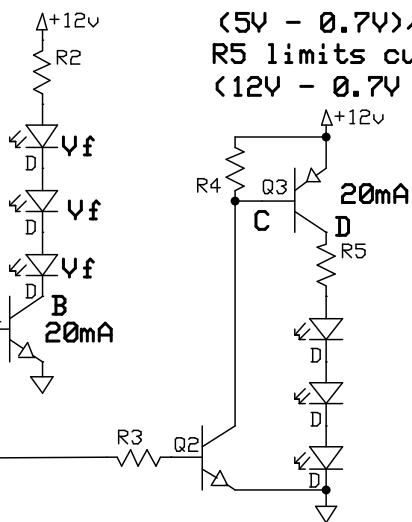
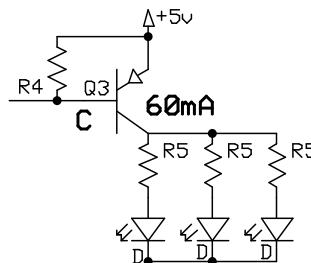


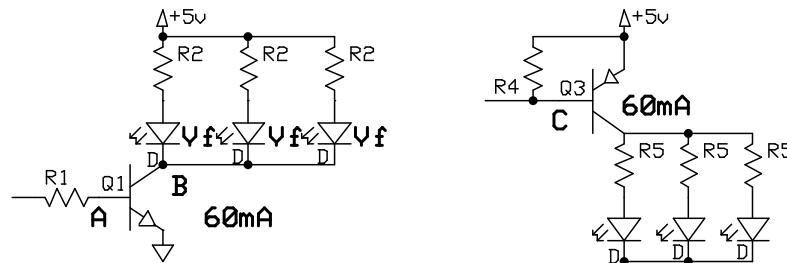NPN Q1 - Arduino High supplies current to Q1,
 Q1 turns on to allow current flow thru LEDs.
 Voltage at A and B will be ~0.7V.
 R1 limits current from Arduino into Q1:
 $(5V - 0.7V) / .020A = 215 \text{ ohm}$
 R2 limits current from 12V into the LEDs:
 $(12V - V_f - V_f - V_f - 0.7V) / .020A = R2 \text{ ohm}$



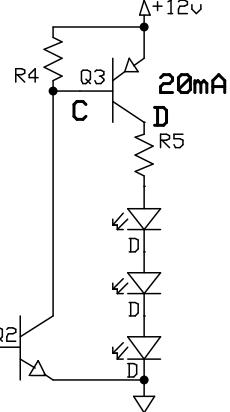PNP Q3 - R4 holds Q3 base high to keep Q3 off.
 Arduino High supplies current to Q2 base,
 Q3 turns on to allow current flow thru LEDs.
 Voltage at C will be ~0.7V and D ~11.3V.
 R3 limits current from Arduino into Q2:
 $(5V - 0.7V) / .020A = 215 \text{ ohm}$
 R5 limits current from 12V into the LEDs:
 $(12V - 0.7V - V_f - V_f - V_f) / .020A = R2 \text{ ohm}$



Alternate methods to drive multiple LEDs